

James C., Meshal, and Kyle Y.

## Building a Circuit

- 6. If we connected a  $1\Omega$  resistor between these two rows - so that it is in a closed loop with the 5V supply from the Rpi, how much current would this circuit attempt to draw across the resistor? **We expect the circuit to have a current of 5 Amps across the resistor**
  - a. The Rpi adaptor provides 5V and up to 2 Amps, is this current sufficient? **It is not sufficient as the circuit will draw more current than the power adaptor will allow for**
  - b. What do you think might happen? Please don't actually do this. **This will not only break through the power adaptor but also cause the resistor to burn up as it pulls way too much current**
- 7. Connect a resistor of more than at least  $100\Omega$  (Why might this be enough resistance?) **This would mean the circuit would only pull 50 mA or less which is considerably less and does not break the resistor**
  - a. If you have a multi-meter able to measure current, evaluate the current across the resistor, is it what you expected? **With a resistor of 120 Ohms, we measured a current that continued to fluctuate but we should have had a current of 41 mA. This is likely due to unstable connections and human error with the board**
    - i. NOTE: to measure current, you have to put the meter in series with the rest of the circuit – it cannot measure current like it would voltage (connecting leads to +/- side of a component) – the current has to run through the meter

## LED in a Circuit

1. Add an LED to your circuit
  - a. Put it in series with the resistor and move the +/- connectors to the RPi 5V supply as needed **Done**
    - i. How does the diode need to be oriented? Which wire on the LED goes to the +5V side and which goes to the GND connector? **It needs to be oriented so that the positive side goes toward the 5V side and the cathode goes towards the GND connector. This way, current flows through it**
  - b. What is the voltage drop across the resistor? Was this what you expected? **We found it was 2.88 V. which fit our expectations**
  - c. What is the voltage drop across the LED? **It was about 2.12 V which matches since the total voltage drop should be -5 V**
2. Try removing the resistor from the circuit, keeping the circuit closed - the LED is just in series with the 5V supply.
  - a. What do you think will happen to the LED brightness? **It should be brighter since the brightness is determined by the current flowing through it unless the current is too much and the diode stops behaving like a diode.**
3. Try including resistors of different values - how does LED brightness change vs resistor strength? **As the Resistor increases in strength, the LED gets darker**
  - a. Do the voltage drops across the resistors and LED change? **Yes they do, the voltage drop across the resistor is bigger, and it is smaller across the LED**
4. Using the configuration with the highest LED brightness now move the 5V connection on the RPi to one of the 3.3V pins.
  - a. What do you expect to happen to the LED brightness? **We expect it to get darker since the Voltage drop across the LED gets smaller as the voltage of the power supply decreases.**
5. Add a step-up circuit components to increase your RPi voltage from 5V to 10V but do not close your circuit yet
  - a. Using the dimmest configuration for the LED explored previously (meaning select the appropriate resistor from those you tried previously) now
  - b. How will the LED brightness change? **It increased in brightness compared to the 5V power supply with the higher resistor**
6. How would you quantify the LED brightness changes? **LED Brightness changes proportionally to the voltage drop across it.**
7. Do any of these results change with different color LEDs? Specifically do any voltage drop values change, is the relative brightness similar for different color LEDs, etc. **It depends on the rating of the bulb, but it is brighter for bulbs that have higher internal resistance**

## Photo Diode

- 1. Replace the LED with a photo-diode (remove the step-up component as well if you had one included previously)
  - a. NOTE: photo-diodes operate in reverse bias mode so you will need to orient the diode accordingly
- 2. What is the voltage across the resistor when you simply connect the 5V supply to close this circuit?
  - **The voltage around the resistor is close to 0.45 V**
- 3. What happens if you cover the photo-diode? What happens if you change the +connector to go to the 3.3V pin on the Rpi? **When we cover the photo-diode, we see the voltage drop significantly. We see similar effects when we lower the voltage**
- a. What is the dark current for this photo-diode? (Use the voltage across the resistor to determine diode current)
  - **We find the dark current to be 0.00212 mA**
- b. Is 5V enough supply voltage to see a signal from this diode? Is 3.3V?
  - **We found 5V to be enough to see a signal but found that 3.3 was barely enough to find anything**
- c. What happens if you attach the step-up circuit component to increase the supply up to 10V?
  - **After attaching the 10V, we still saw a very small voltage drop across the resistor**
- 4. What are the dark current and saturation current for the photo-diode?
  - **We found the dark current to be 0.002mA and the saturation current to be 1.9 mA across the circuit**